


SN74HC595 drives 4-digit digital tube Experiment

74HC595 Introduction

The 74HC595 is a CMOS shift register containing 8-bit serial input and parallel open-drain output that provides data to a register with three-state output. Shift register and storage register, respectively, have an independent clock respectively, the shift register 74 hc595 are needed with the highest priority (SRCLR) directly in the end, serial input (DS) used to cascade of serial output at the next higher level, when the output enable (OE) is a high end, 74 hc595 are needed in parallel in a high impedance state, output for the low level is enabled for parallel output.

Both the shift register clock SHCP and the storage register clock STCP are raised edge triggers.

Pinning information

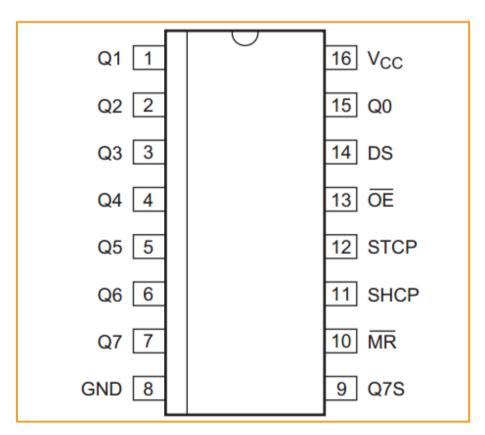



Pin description

Symbol	Pin	Description
Q0	15	parallel data output 0
Q1	1	parallel data output 1
Q2	2	parallel data output 2
Q3	3	parallel data output 3
Q4	4	parallel data output 4
Q5	5	parallel data output 5
Q6	6	parallel data output 6
Q7	7	parallel data output 7
GND	8	ground(0V)
Q7S	9	serial data output
MR	10	master reset(active low)
SHCP	11	shift register clock input
STCP	12	storage register clock input
OE	13	output enable input(active low)
DS	14	serial data input
Vcc	16	supply voltage

Experiment Purpose


In this experiment, we used Arduino to drive the serial output to 74HC595, and then the parallel port of 74HC595 to drive a common cathode four-digit digital tube. Then driven directly by the Arduino digital tube of a foot, this experiment using eight 220 Ω resistance limit current role, let the dynamic display of digital tube digital has been reduced to 0 from 9.

Component List

- Keywish Arduino UNO R3 mainboard
- 4-7Segment cathode tube * 1
- ◆ SN74HC595 * 1
- 220 Ω resistor* 8
- Several jumper wires



Schematic Diagram

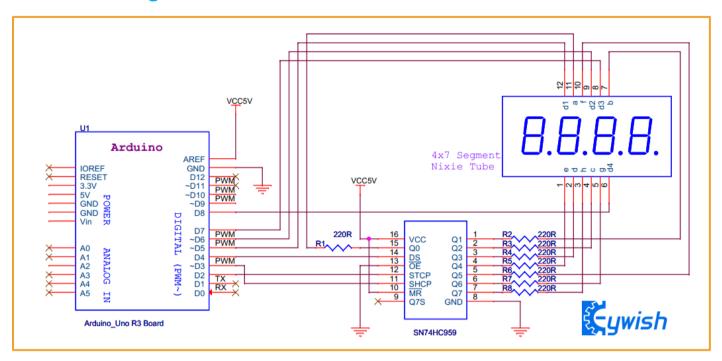


Wiring of Circuit

arduino Uno	SN74HC595
2	12(STCP)
3	11(SHCP)
4	14(DS)

arduino Uno	7 Segment nixie tube
5	12
6	9
7	8
8	6

SN74HC595	7 Segment nixie tube
15	11
1	7
2	5
3	2
4	1
5	10
6	5
7	3



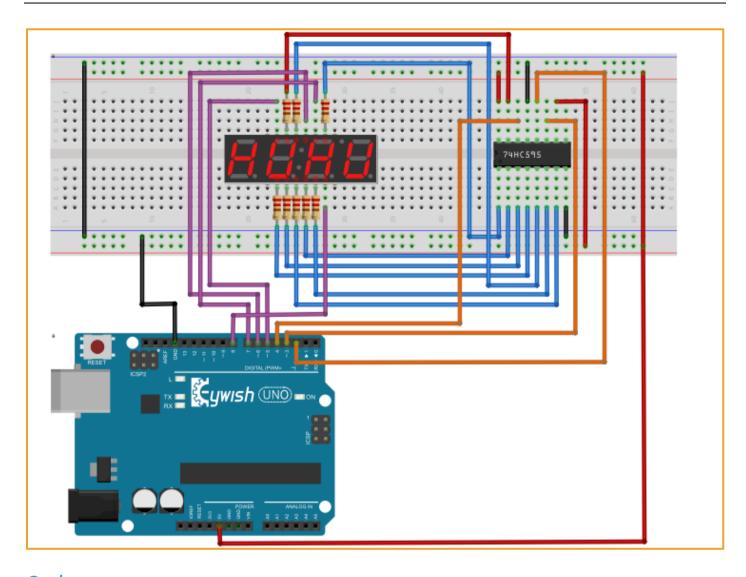

Code


```
#define BIT_CHOICE_1 5
#define BIT_CHOICE_2 6
#define BIT_CHOICE_3 7
#define BIT_CHOICE_4 8
#define STCP_PIN 2
#define SHCP_PIN 3
#define DATA_PIN 4 / Define the stcp shcp ds pin
int BIT_CHOICE[4]= {BIT_CHOICE_1 , BIT_CHOICE_2 ,BIT_CHOICE_3,BIT_CHOICE_4};// 4x8bit
unsigned char DisplayNumble[10]=
{0xC0,0x90,0x80,0x88,0x82,0x92,0x99,0x80,0x44,0xF9};
```



```
void setup()
   pinMode(STCP PIN, OUTPUT);
   pinMode(SHCP PIN, OUTPUT);
   pinMode (DATA PIN, OUTPUT); // Set the stcp shcp ds pin to output mode
   for (int i=0;i<4;i++)</pre>
       pinMode(BIT CHOICE[i], OUTPUT);
        digitalWrite(BIT CHOICE[i], HIGH);
   }
}
void loop()
   int i=0;
   for (i = 9; i>=0 ;i--)
   // numble 9-> 0 down Cycle 9 times, cycle to light up segment eight segment digital
   tube belt and dot
       for (int i=0;i<4;i++)</pre>
           digitalWrite(BIT CHOICE[i], HIGH);
       digitalWrite(STCP PIN, LOW);
       shiftOut(DATA PIN,SHCP PIN,MSBFIRST, DisplayNumble[i]);
           // Move left to display numbers
       digitalWrite(STCP_PIN, HIGH);
       for(int i=0;i<4; i++)</pre>
       {
           digitalWrite(BIT CHOICE[i], LOW);
       delay(1000); // Delay for one second
   }
```



Experiment Result

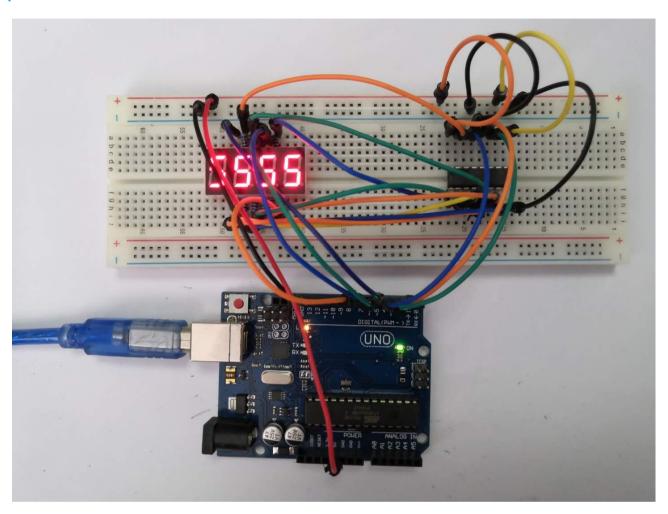

Mixly programming program



MagicBlock programming program

